

1. (35 points) A dielectric filled rectangular waveguide has the following characteristics:

$$b = 1.5 \text{ cm}, a = 3.0 \text{ cm}, \mu_r = 1 \text{ and } \epsilon_r = 2.25.$$


Calculate the lowest cut-off frequency for the guide. Also determine λ_g , the guide wavelength at 4.0 GHz.

2. (30 points) An air filled rectangular waveguide has $a = 5 \text{ cm}$ and $b = 2 \text{ cm}$. Determine if TM_{21} mode is evanescent at 8 GHz. If the mode is evanescent, find the attenuation constant; if not, find the phase constant and phase velocity for this mode.

3. (35 points) A plane wave at 2 GHz, in free space, is normally incident on a half space of copper. The conductivity of copper is $5.7 \times 10^7 \text{ S/m}$. Compute the reflection and transmission coefficients. Also determine the depth at which the fields in copper would be attenuated by 30 dB.


1. (35 points) A microstrip line operating at 2.5 GHz has a dielectric substrate of $\epsilon_r = 2.20$. The effective dielectric constant, ϵ_e for the microstrip geometry is measured as 1.87. Also, an approximate electrostatic solution is used to determine that the capacitance should be 91.2 pF/m. Determine the numerical values for the propagation constant, β and the characteristic impedance, Z_0 for this microstrip.

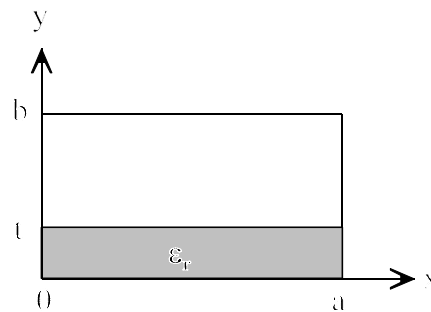2. (30 points) Use the transverse resonance technique to derive a transcendental equation(s) for the propagation constant of the TE_{0n} modes of a rectangular waveguide that is dielectric filled from $0 < y < t$ and air filled from $t < y < b$. Do not solve the equation(s).



3. (35 points) Consider a circular waveguide with $a = 0.75$ cm, air filled for $z < 0$ and dielectric filled ($\epsilon_r = 2.25$) for $z > 0$. If the operating frequency is 13.0 GHz, use an equivalent transmission line model to compute the reflection coefficient, Γ of a TE_{11} wave that is incident on the interface from $z < 0$.

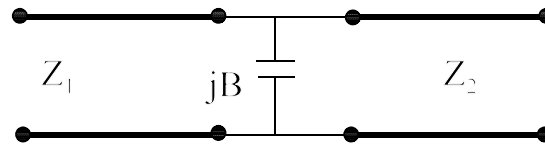1. (25 points) Determine the maximum power handling capacity of a WR-137 rectangular waveguide of dimension 3.485×1.580 cm and operating at 7.5 GHz in a TE_{10} mode. The electrical breakdown for air is 3 MV/m. Assume the waveguide is matched ($VSWR = 1.0$).
2. (30 points) Design a two-section Chebyshev quarter-wave impedance transformer to match a 40Ω line to a 100Ω load. The maximum permissible VSWR over the pass band is 1.2. What is the resulting bandwidth?
3. (20 points) Consider an air filled circular waveguide with $a = 2.0$ cm. What is the cut-off frequency of the guide for TM_{11} mode? This waveguide is used to form a cavity to resonate in TM_{111} mode at 10.5 GHz. Find the dimensions of the cavity.
4. (25 points) An equivalent circuit for a change in the height of a rectangular waveguide is shown below. Find the scattering matrix for the two-port network shown.




$$Z_1 = 100 \Omega, Z_2 = 200 \Omega \text{ and } B = 0.05 \text{ S.}$$

Useful Formulas:

$$\cosh^{-1} x = \ln \left(x + \sqrt{x^2 - 1} \right)$$

$$\cosh x = \frac{e^x + e^{-x}}{2}$$

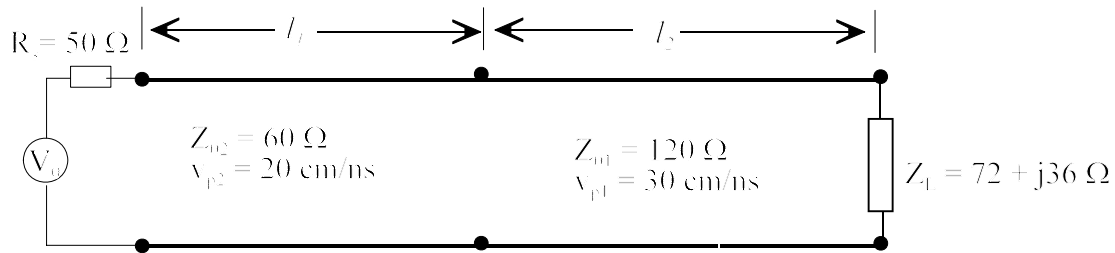1. (20 points) For the transmission line system shown below, assuming both lines are lossless and assuming a source voltage $V_0 = 100 e^{j0} \text{ V @ } 100 \text{ MHz}$, find the input impedance of the line and the time average power delivered to the load. Note that $l_1 = 3.75 \text{ m}$ and $l_2 = 1.75 \text{ m}$.



Name _____

Spring 2006

EECS 320

Exam 2

2. (20 points) A transmission line model of an IC interconnect at 5 GHz is found to have following parameters: $R = 143.5 \Omega/\text{cm}$, $L = 10.1 \text{ nH}/\text{cm}$, $C = 1.1 \text{ pF}/\text{cm}$ and $G = 0.014 \text{ S}/\text{cm}$. Determine the propagation constant β , attenuation α in dB/cm, characteristic impedance Z_0 , velocity of propagation v_p , and wavelength λ_g in cm.

Name _____


Spring 2006

EECS 320

Exam 2

3. (20 points) A 50Ω transmission line is terminated with an antenna (load) having a feed point impedance of 150Ω . Calculate V_{\max} , V_{\min} , I_{\max} , I_{\min} , Z_{\max} , Z_{\min} along the line. Assume $V^+ = 5 \text{ V}$ and $\lambda = 15 \text{ cm}$.

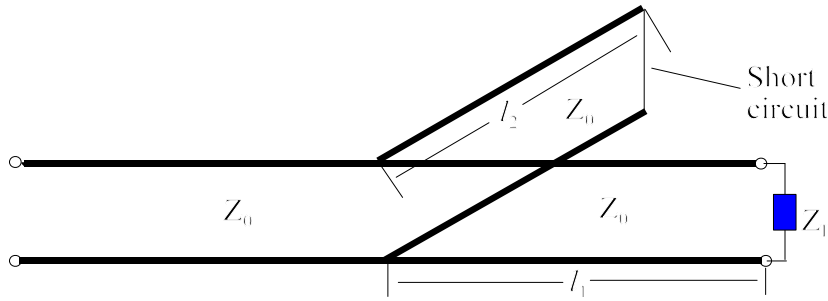1. (20 points) Design a single stub tuner that will match a 100Ω lossless, coaxial cable to an antenna with an input impedance of $Z_L = 300 - j 100 \Omega$. Choose the design that locates the stub closest to the antenna.



Name: _____

ECE 320

Spring 2006
Final Exam

2. (10 points) The S-parameters for a certain two-port network are

$$s_{11} = 0.26 - j0.16, s_{12} = s_{21} = 0.42, s_{22} = 0.36 - j0.57.$$

Determine the input reflection coefficient of the two-port when $Z_L = 3Z_0$.


Name: _____

ECE 320


Spring 2006
Final Exam

3. (15 points) Design a two section quarter wave transformer to match a load of $Z_L = 300 \Omega$ to a line with $Z_0 = 50 \Omega$ line and to operate at 250 MHz. Assume the lines have velocity of propagation to be 250 Mm/s. Your design must specify the characteristic impedances and the line lengths in cm.

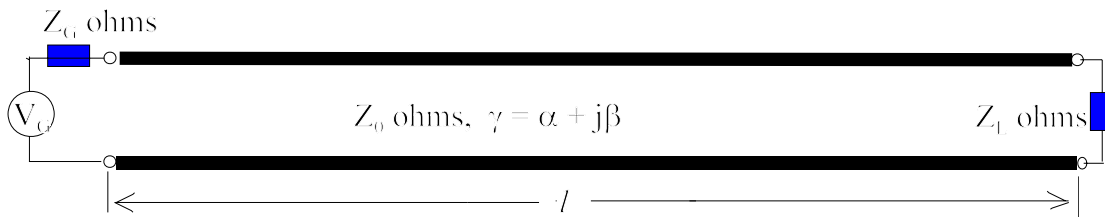4. (15 points) Determine the power delivered by the source to the load. Note that $\alpha = 1.0$ dB/km, $\beta = 0.0182$ rad/meter, and $Z_0 = 50 \Omega$, $Z_G = Z_L = 50 \Omega$. The line is 1 km long and the source voltage is 110 V rms.



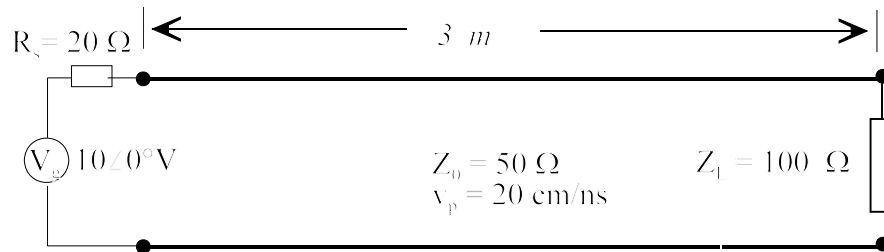5. (20 points) A sinusoidal voltage source of 10 V (rms) and $R_s = 20 \Omega$ is connected to a load impedance $Z_L = 100 \Omega$ through a 3-m long, lossless coaxial transmission line filled with polyethylene ($v_p = 20$ cm/ns at 25 MHz) and with $Z_0 = 50 \Omega$ as shown. Find the voltage and current at the load with reference to the source voltage.



6. (20 points) A Time Domain Reflectometer (TDR) is used to test the transmission line system shown below. The TDR scope display of $v_s(t)$ is also shown. Determine the values of Z_{01} , l_1 and R_1 . Assume the propagation velocity to be 2×10^8 m/s.

