



## Some examples



**Paolo PRINETTO**  
 Politecnico di Torino (Italy)  
 University of Illinois at Chicago, IL (USA)

Paolo.Prinetto@polito.it  
 Prinetto@uic.edu  
 www.testgroup.polito.it

### Goal

- This lecture guides the students through the solution of some simple examples of manual synthesis of combinational networks.

6.3

2

### Prerequisites

- Lectures 6.1 and 6.2

6.3

3

### Homework

- Students are recommended to try to solve the exercise by themselves, before looking at the proposed solutions.

6.3

4

### Further readings

- No particular suggestion

6.3

5



### Exercise #6.3.1

Design a combinational circuit with 1 output  $U$  and an input  $X$  (3 downto 0) that, when it receives on  $X$  an unsigned *hexadecimal* digit  $X$ , provides, on  $U$ , a logical value 1 iff:

$$X < 4 \text{ or } X > 8.$$

6.3

6

**Solution #1**

- We are going to present a complete first solution, i.e., till the netlist of the target circuit.

6.3 7

**Solution #1**

|        |        |        |        |    |    |
|--------|--------|--------|--------|----|----|
|        |        | $X(3)$ | $X(2)$ |    |    |
| $X(1)$ | $X(0)$ | 00     | 01     | 11 | 10 |
| 00     |        |        |        |    |    |
| 01     |        |        |        |    |    |
| 11     |        |        |        |    |    |
| 10     |        |        |        |    |    |

**U**

6.3 8

**Solution #1**

|        |        |        |        |    |    |
|--------|--------|--------|--------|----|----|
|        |        | $X(3)$ | $X(2)$ |    |    |
| $X(1)$ | $X(0)$ | 00     | 01     | 11 | 10 |
| 00     |        |        |        |    |    |
| 01     |        |        |        |    |    |
| 11     |        |        |        |    |    |
| 10     |        |        |        |    |    |

**HINT:**  
label each cell with its corresponding decimal value

6.3 9

**Solution #1**

|        |        |        |        |    |    |
|--------|--------|--------|--------|----|----|
|        |        | $X(3)$ | $X(2)$ |    |    |
| $X(1)$ | $X(0)$ | 00     | 01     | 11 | 10 |
| 00     |        | 0      | 4      | 12 | 8  |
| 01     |        | 1      | 5      | 13 | 9  |
| 11     |        | 3      | 7      | 15 | 11 |
| 10     |        | 2      | 6      | 14 | 10 |

**U**

6.3 10

**Solution #1**

$X < 4$  or  $X > 8$ .

|        |        |                |        |                 |    |
|--------|--------|----------------|--------|-----------------|----|
|        |        | $X(3)$         | $X(2)$ |                 |    |
| $X(1)$ | $X(0)$ | 00             | 01     | 11              | 10 |
| 00     |        | 1 <sub>0</sub> | 4      | 1 <sub>12</sub> | 8  |
| 01     |        | 1 <sub>1</sub> | 5      | 1 <sub>13</sub> | 9  |
| 11     |        | 1 <sub>3</sub> | 7      | 1 <sub>15</sub> | 11 |
| 10     |        | 1 <sub>2</sub> | 6      | 1 <sub>14</sub> | 10 |

**U**

6.3 11







**Solution #1**







$X < 4$  or  $X > 8$ .

|        |        |                |        |                 |    |
|--------|--------|----------------|--------|-----------------|----|
|        |        | $X(3)$         | $X(2)$ |                 |    |
| $X(1)$ | $X(0)$ | 00             | 01     | 11              | 10 |
| 00     |        | 1 <sub>0</sub> | 4      | 1 <sub>12</sub> | 8  |
| 01     |        | 1 <sub>1</sub> | 5      | 1 <sub>13</sub> | 9  |
| 11     |        | 1 <sub>3</sub> | 7      | 1 <sub>15</sub> | 11 |
| 10     |        | 1 <sub>2</sub> | 6      | 1 <sub>14</sub> | 10 |

**U**

6.3 12

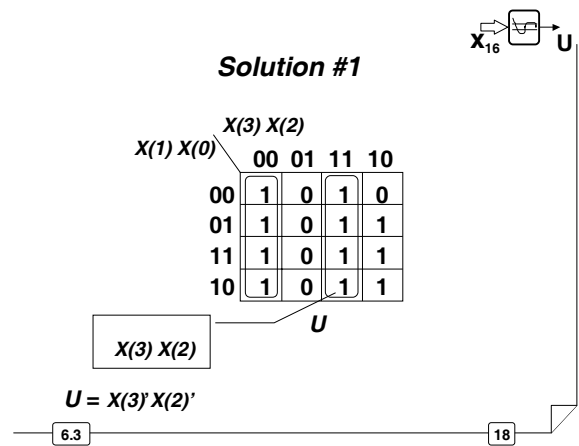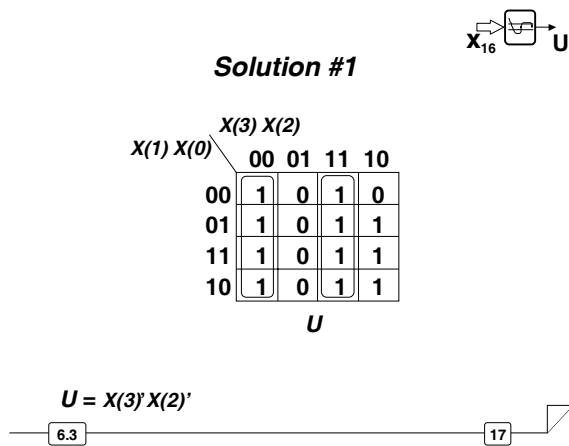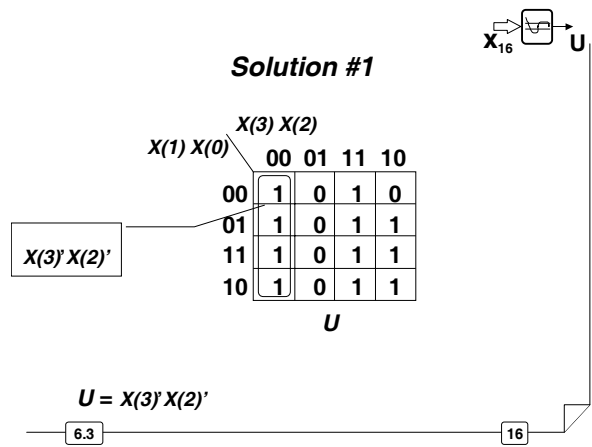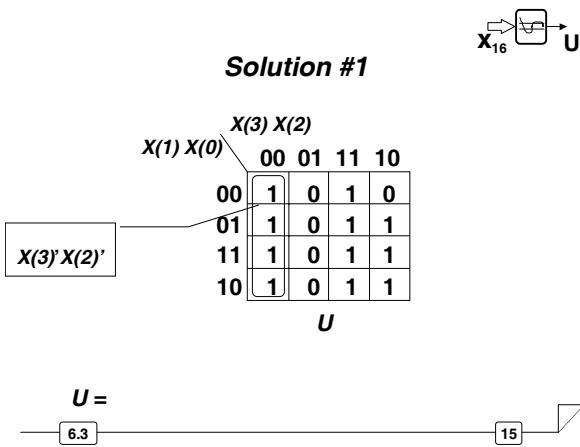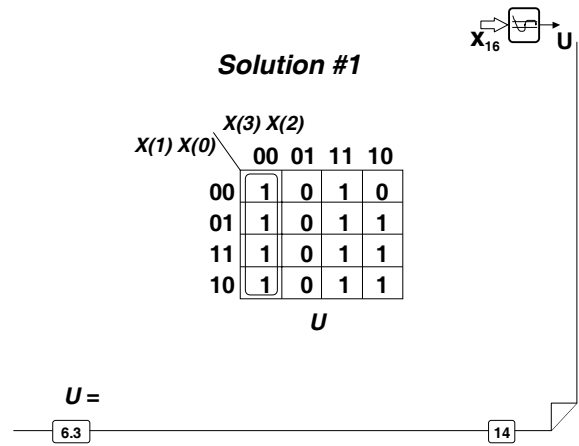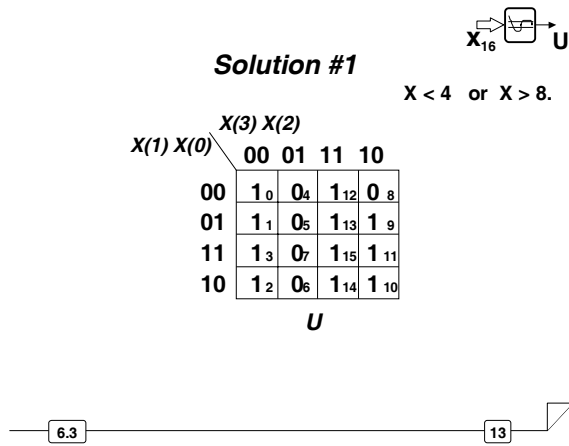

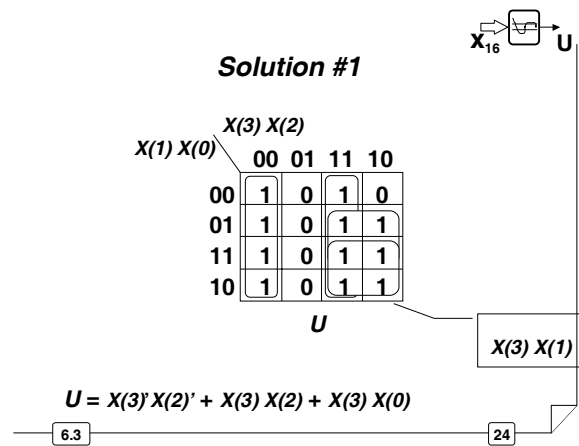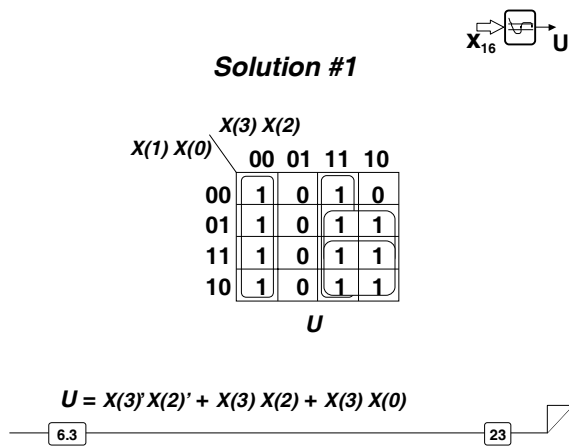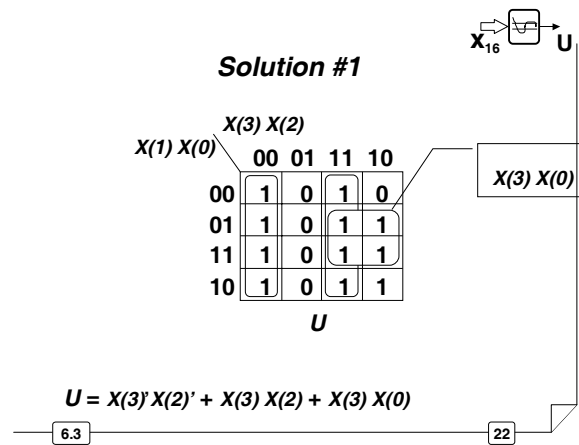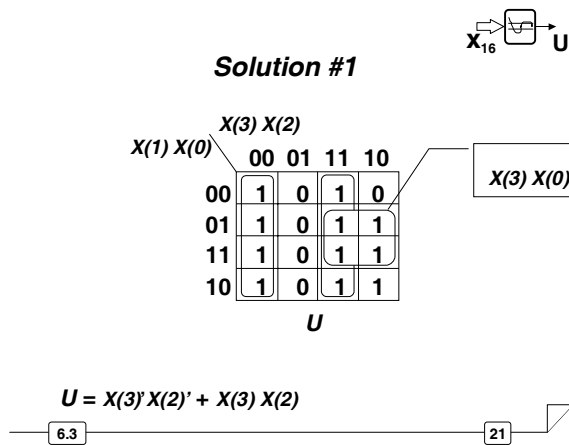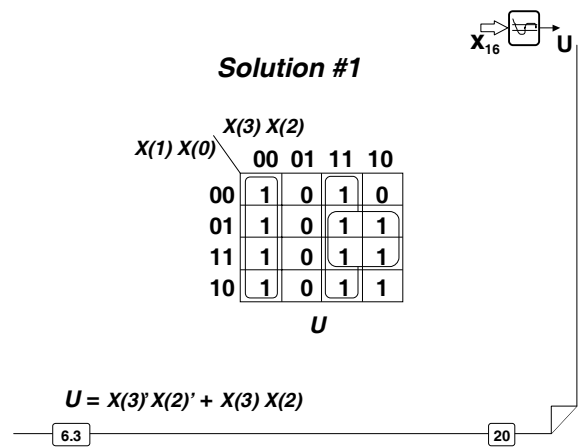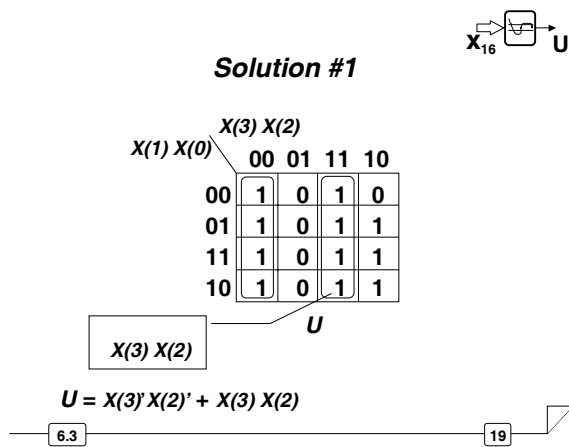

**Solution #1**

|             |             |    |    |    |
|-------------|-------------|----|----|----|
|             | $X(3) X(2)$ |    |    |    |
| $X(1) X(0)$ | 00          | 01 | 11 | 10 |
| 00          | 1           | 0  | 1  | 0  |
| 01          | 1           | 0  | 1  | 1  |
| 11          | 1           | 0  | 1  | 1  |
| 10          | 1           | 0  | 1  | 1  |

$U$

$X(3) X(1)$

$U = X(3)' X(2)' + X(3) X(2) + X(3) X(0) + X(3) X(1)$

6.3 25

**Solution #1**

$U = X(3)' X(2)' + X(3) X(2) + X(3) X(0) + X(3) X(1)$

6.3 26

**Solution #1**

$U = X(3)' X(2)' + X(3) X(2) + X(3) X(0) + X(3) X(1)$

6.3 27

**Solution #1**

Further optimization:

- by observing that:

- one gets:

6.3 28







**Solution #1**

6.3 29

**Solution #2**

- We are going to present now an alternative solution, due to a different cover of the K-map of the circuit.

6.3 30

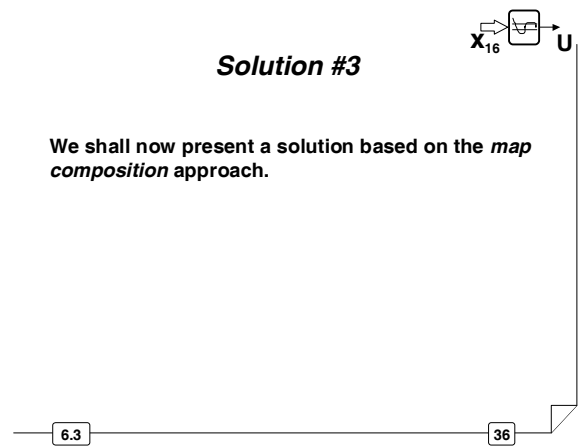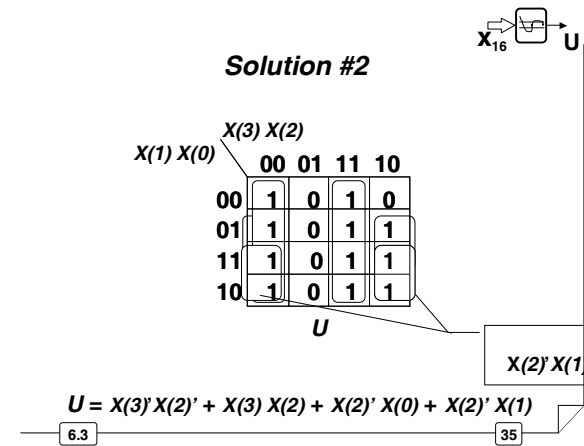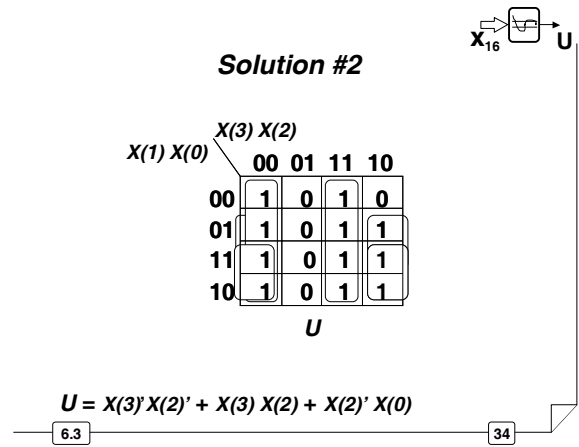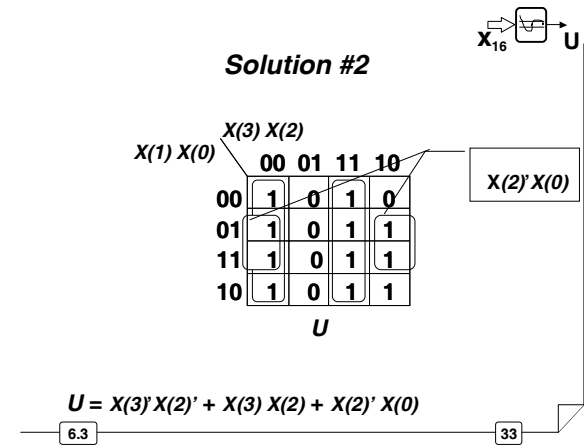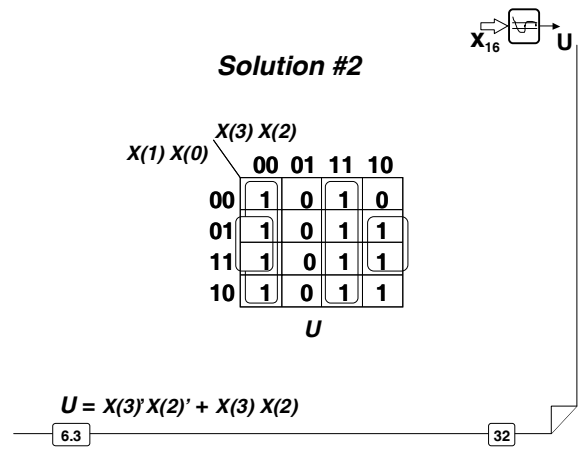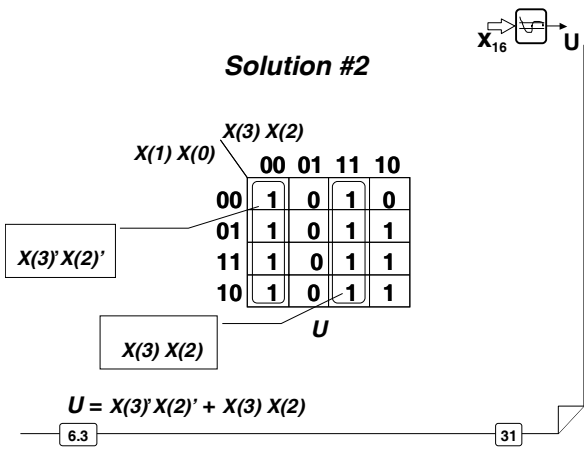

$X(3) X(2) X(1) X(0) \equiv abcd$

**Solution #3**

|    |    |    |    |    |   |
|----|----|----|----|----|---|
|    | ab |    |    |    |   |
| cd | 00 | 01 | 11 | 10 |   |
| 00 | 1  | 0  | 1  | 0  |   |
| 01 | 1  | 0  | 1  | 1  |   |
| 11 | 1  | 0  | 1  | 1  |   |
| 10 | 1  | 0  | 1  | 1  |   |
|    |    |    |    |    | f |

$f =$

6.3

37



**Solution #3**

|    |    |    |    |    |   |
|----|----|----|----|----|---|
|    | ab |    |    |    |   |
| cd | 00 | 01 | 11 | 10 |   |
| 00 | 1  | 0  | 1  | 0  |   |
| 01 | 1  | 0  | 1  | 1  |   |
| 11 | 1  | 0  | 1  | 1  |   |
| 10 | 1  | 0  | 1  | 1  |   |
|    |    |    |    |    | f |


|    |    |    |    |    |   |
|----|----|----|----|----|---|
|    | ab |    |    |    |   |
| cd | 00 | 01 | 11 | 10 |   |
| 00 | 1  | 0  | 1  | 0  |   |
| 01 | 1  | 0  | 1  | 0  |   |
| 11 | 1  | 0  | 1  | 0  |   |
| 10 | 1  | 0  | 1  | 0  |   |
|    |    |    |    |    | E |

|    |    |    |    |    |   |
|----|----|----|----|----|---|
|    | ab |    |    |    |   |
| cd | 00 | 01 | 11 | 10 |   |
| 00 | -  | 0  | -  | 0  |   |
| 01 | -  | 0  | -  | 1  |   |
| 11 | -  | 0  | -  | 1  |   |
| 10 | -  | 0  | -  | 1  |   |
|    |    |    |    |    | R |

$f = E + R$

6.3

38

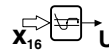

**Solution #3**

|    |    |    |    |    |   |
|----|----|----|----|----|---|
|    | ab |    |    |    |   |
| cd | 00 | 01 | 11 | 10 |   |
| 00 | 1  | 0  | 1  | 0  |   |
| 01 | 1  | 0  | 1  | 1  |   |
| 11 | 1  | 0  | 1  | 1  |   |
| 10 | 1  | 0  | 1  | 1  |   |
|    |    |    |    |    | f |

|    |    |    |    |    |   |
|----|----|----|----|----|---|
|    | ab |    |    |    |   |
| cd | 00 | 01 | 11 | 10 |   |
| 00 | 1  | 0  | 1  | 0  |   |
| 01 | 1  | 0  | 1  | 0  |   |
| 11 | 1  | 0  | 1  | 0  |   |
| 10 | 1  | 0  | 1  | 0  |   |
|    |    |    |    |    | E |


|    |    |    |    |    |   |
|----|----|----|----|----|---|
|    | ab |    |    |    |   |
| cd | 00 | 01 | 11 | 10 |   |
| 00 | -  | 0  | -  | 0  |   |
| 01 | -  | 0  | -  | 1  |   |
| 11 | -  | 0  | -  | 1  |   |
| 10 | -  | 0  | -  | 1  |   |
|    |    |    |    |    | R |

$E = a'b' + ab = (a \oplus b)'$   
 $R = ad + ac$

$f = E + R$

6.3

39

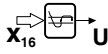

**Solution #3**

|    |    |    |    |    |   |
|----|----|----|----|----|---|
|    | ab |    |    |    |   |
| cd | 00 | 01 | 11 | 10 |   |
| 00 | 1  | 0  | 1  | 0  |   |
| 01 | 1  | 0  | 1  | 1  |   |
| 11 | 1  | 0  | 1  | 1  |   |
| 10 | 1  | 0  | 1  | 1  |   |
|    |    |    |    |    | f |

|    |    |    |    |    |   |
|----|----|----|----|----|---|
|    | ab |    |    |    |   |
| cd | 00 | 01 | 11 | 10 |   |
| 00 | 1  | 0  | 1  | 0  |   |
| 01 | 1  | 0  | 1  | 0  |   |
| 11 | 1  | 0  | 1  | 0  |   |
| 10 | 1  | 0  | 1  | 0  |   |
|    |    |    |    |    | E |

|    |    |    |    |    |   |
|----|----|----|----|----|---|
|    | ab |    |    |    |   |
| cd | 00 | 01 | 11 | 10 |   |
| 00 | -  | 0  | -  | 0  |   |
| 01 | -  | 0  | -  | 1  |   |
| 11 | -  | 0  | -  | 1  |   |
| 10 | -  | 0  | -  | 1  |   |
|    |    |    |    |    | R |

$E = a'b' + ab = (a \oplus b)'$   
 $R = ad + ac$

$f = E + R = a'b' + ab + ad + ac$

6.3

40



**Exercise #6.3.2**

Design a combinational circuit with a 4-bit input and a 3-bit output such that, when it receives on its input a hexadecimal digit X, provides, on its output:

$\lceil \text{sqrt}(X) \rceil$

6.3

41




**Solution #1 (truth table)**


| A | B | C | D | $\lceil \text{sqrt}(X) \rceil$ |
|---|---|---|---|--------------------------------|
| 0 | 0 | 0 | 0 | 0 0 0                          |
| 0 | 0 | 0 | 1 | 0 0 1                          |
| 0 | 0 | 1 | 0 | 0 1 0                          |
| 0 | 0 | 1 | 1 | 0 1 0                          |
| 0 | 1 | 0 | 0 | 0 1 0                          |
| 0 | 1 | 0 | 1 | 0 1 1                          |
| 0 | 1 | 1 | 0 | 0 1 1                          |
| 0 | 1 | 1 | 1 | 0 1 1                          |
| 1 | 0 | 0 | 0 | 0 1 1                          |
| 1 | 0 | 0 | 1 | 0 1 1                          |
| 1 | 0 | 1 | 0 | 1 0 0                          |
| 1 | 0 | 1 | 1 | 1 0 0                          |
| 1 | 1 | 0 | 0 | 1 0 0                          |
| 1 | 1 | 0 | 1 | 1 0 0                          |
| 1 | 1 | 1 | 0 | 1 0 0                          |
| 1 | 1 | 1 | 1 | 1 0 0                          |

6.3

42

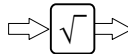

**Solution #1 (Karnaugh maps)**

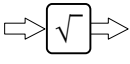

|    |    |    |    |    |
|----|----|----|----|----|
| AB | 00 | 01 | 11 | 10 |
| CD | 00 | 0  | 1  | 0  |
|    | 01 | 0  | 1  | 0  |
|    | 11 | 0  | 1  | 1  |
|    | 10 | 0  | 1  | 1  |

|    |    |    |    |    |
|----|----|----|----|----|
| AB | 00 | 01 | 11 | 10 |
| CD | 00 | 0  | 1  | 0  |
|    | 01 | 0  | 1  | 0  |
|    | 11 | 1  | 1  | 0  |
|    | 10 | 1  | 1  | 0  |

|    |    |    |    |    |
|----|----|----|----|----|
| AB | 00 | 01 | 11 | 10 |
| CD | 00 | 0  | 0  | 0  |
|    | 01 | 1  | 1  | 0  |
|    | 11 | 0  | 1  | 0  |
|    | 10 | 0  | 1  | 0  |

[ sqrt (X) ]

6.3

43


**Exercise #6.3.3**

Similar to the example #1, with the only difference that the input digit X is, in this case, a *decimal* one.

6.3

44

**Solution #1**

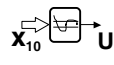


|             |    |    |    |    |
|-------------|----|----|----|----|
| $X(3) X(2)$ | 00 | 01 | 11 | 10 |
| $X(1) X(0)$ | 00 | 0  | 4  | 12 |
|             | 01 | 1  | 5  | 13 |
|             | 11 | 3  | 7  | 15 |
|             | 10 | 2  | 6  | 14 |

$U$

6.3

45

**Solution #1**

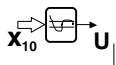


|             |    |                |                |     |
|-------------|----|----------------|----------------|-----|
| $X(3) X(2)$ | 00 | 01             | 11             | 10  |
| $X(1) X(0)$ | 00 | 1 <sub>0</sub> | 0 <sub>4</sub> | -12 |
|             | 01 | 1 <sub>1</sub> | 0 <sub>5</sub> | -13 |
|             | 11 | 1 <sub>3</sub> | 0              | -15 |
|             | 10 | 1 <sub>2</sub> | 0 <sub>6</sub> | -14 |

$U$

6.3

46

**Solution #1**

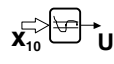

|             |    |    |    |    |
|-------------|----|----|----|----|
| $X(3) X(2)$ | 00 | 01 | 11 | 10 |
| $X(1) X(0)$ | 00 | 1  | 0  | -  |
|             | 01 | 1  | 0  | -  |
|             | 11 | 1  | 0  | -  |
|             | 10 | 1  | 0  | -  |


$U$

$U = X(3)' X(2)'$

6.3

47

**Solution #1**



|             |    |    |    |    |
|-------------|----|----|----|----|
| $X(3) X(2)$ | 00 | 01 | 11 | 10 |
| $X(1) X(0)$ | 00 | 1  | 0  | -  |
|             | 01 | 1  | 0  | -  |
|             | 11 | 1  | 0  | -  |
|             | 10 | 1  | 0  | -  |

$U$

$U = X(3)' X(2)' + X(3) X(0)$

6.3

48

**Solution #1**

$U = X(3)'X(2)' + X(3)X(0)$

6.3 49

**Solution #2**

|             |           |           |    |    |    |
|-------------|-----------|-----------|----|----|----|
|             |           | X(3) X(2) |    |    |    |
|             | X(1) X(0) | 00        | 01 | 11 | 10 |
| X(3)' X(2)' | 00        | 1         | 0  | -  | 0  |
|             | 01        | 1         | 0  | -  | 1  |
|             | 11        | 1         | 0  | -  | -  |
|             | 10        | 1         | 0  | -  | -  |

$U = X(3)'X(2)'$

6.3 50

**Solution #2**

|             |           |           |    |    |    |
|-------------|-----------|-----------|----|----|----|
|             |           | X(3) X(2) |    |    |    |
|             | X(1) X(0) | 00        | 01 | 11 | 10 |
| X(3)' X(2)' | 00        | 1         | 0  | -  | 0  |
|             | 01        | 1         | 0  | -  | 1  |
|             | 11        | 1         | 0  | -  | -  |
|             | 10        | 1         | 0  | -  | -  |

$U = X(3)'X(2)' + X(2)'X(0)$

6.3 51

**Exercise #6.3.4**

Design a comparator which, receiving in input:

- A (1 downto 0) and B (1 downto 0)
- a signal  $2C/\sim UM$  specifying the coding used for A and B (1=2's complement, 0=unsigned magnitude)

provides 3 outputs  $A\_GT\_B$ ,  $A\_EQ\_B$  and  $A\_LT\_B$  such that:

- $A\_GT\_B = 1$  iff  $A > B$
- $A\_EQ\_B = 1$  iff  $A = B$
- $A\_LT\_B = 1$  iff  $A < B$ .

6.3 52

**Solution #1**

|  |           |           |    |          |    |
|--|-----------|-----------|----|----------|----|
|  |           | A(1) A(0) |    |          |    |
|  | B(1) B(0) | 2C/~UM=0  |    | 2C/~UM=1 |    |
|  |           | 00        | 01 | 11       | 10 |
|  | 00        |           |    |          |    |
|  | 01        |           |    |          |    |
|  | 11        |           |    |          |    |
|  | 10        |           |    |          |    |
|  |           |           |    |          |    |

6.3 53

**Solution #1**

|  |                               |  |    |          |    |
|--|-------------------------------|--|----|----------|----|
|  |                               | A <sub>1</sub> A <sub>0</sub> 2C/~UM=0 |    | 2C/~UM=1 |    |
|  | B <sub>1</sub> B <sub>0</sub> | 00                                     | 01 | 11       | 10 |
|  | 00                            | 0                                      | 1  | 1        | 1  |
|  | 01                            | 0                                      | 0  | 1        | 1  |
|  | 11                            | 0                                      | 0  | 0        | 0  |
|  | 10                            | 0                                      | 0  | 1        | 0  |
|  |                               |  | 0  | 1        | 0  |

$A\_gt\_B$

6.3 54

**Solution #1**

The implementation of  $A_{eq\_B}$  is trivial:

| $A_1 A_0$ |    | $2C/\sim UM = 0$ |    |    |    | $2C/\sim UM = 1$ |    |    |    |
|-----------|----|------------------|----|----|----|------------------|----|----|----|
|           |    | 00               | 01 | 11 | 10 | 00               | 01 | 11 | 10 |
| $B_1 B_0$ | 00 | 1                | 0  | 0  | 0  | 1                | 0  | 0  | 0  |
|           | 01 | 0                | 1  | 0  | 0  | 0                | 1  | 0  | 0  |
|           | 11 | 0                | 0  | 1  | 0  | 0                | 0  | 1  | 0  |
|           | 10 | 0                | 0  | 0  | 1  | 0                | 0  | 0  | 1  |

$A_{eq\_B}$

6.3

55

**Solution #1**

The 3rd output  $A_{1t\_B}$  can be easily obtained as:

$$A_{1t\_B} = (A_{gt\_B})' (A_{eq\_B})'$$

6.3

56

**Exercise #6.3.5**

Design a combinational circuit with an input  $X$  (2 downto 0) and an output  $Y$  (2 downto 0) such that, when it receives on  $X$  an unsigned *decimal* digit  $X$ , provides, on  $Y$ , the 3 most significant bits of  $X^2$ .

6.3

57

| $X_{(2)}$ | $X_{(10)}$ | $X^2_{(10)}$ | $X^2_{(2)}$ | $Y$ |
|-----------|------------|--------------|-------------|-----|
| 000       |            |              |             |     |
| 001       |            |              |             |     |
| 010       |            |              |             |     |
| 011       |            |              |             |     |
| 100       |            |              |             |     |
| 101       |            |              |             |     |
| 110       |            |              |             |     |
| 111       |            |              |             |     |

6.3

58

| $X_{(2)}$ | $X_{(10)}$ | $X^2_{(10)}$ | $X^2_{(2)}$ | $Y$ |
|-----------|------------|--------------|-------------|-----|
| 000       | 0          |              |             |     |
| 001       | 1          |              |             |     |
| 010       | 2          |              |             |     |
| 011       | 3          |              |             |     |
| 100       | 4          |              |             |     |
| 101       | 5          |              |             |     |
| 110       | 6          |              |             |     |
| 111       | 7          |              |             |     |

6.3

59

| $X_{(2)}$ | $X_{(10)}$ | $X^2_{(10)}$ | $X^2_{(2)}$ | $Y$ |
|-----------|------------|--------------|-------------|-----|
| 000       | 0          | 0            |             |     |
| 001       | 1          | 1            |             |     |
| 010       | 2          | 4            |             |     |
| 011       | 3          | 9            |             |     |
| 100       | 4          | 16           |             |     |
| 101       | 5          | 25           |             |     |
| 110       | 6          | 36           |             |     |
| 111       | 7          | 49           |             |     |

6.3

60

| $X_{(2)}$ | $X_{(10)}$ | $X^2_{(10)}$ | $X^2_{(2)}$ | Y |
|-----------|------------|--------------|-------------|---|
| 000       | 0          | 0            | 000000      |   |
| 001       | 1          | 1            | 000001      |   |
| 010       | 2          | 4            | 000100      |   |
| 011       | 3          | 9            | 001001      |   |
| 100       | 4          | 16           | 010000      |   |
| 101       | 5          | 25           | 011001      |   |
| 110       | 6          | 36           | 100100      |   |
| 111       | 7          | 49           | 110001      |   |

6.3 61

| $X_{(2)}$ | $X_{(10)}$ | $X^2_{(10)}$ | $X^2_{(2)}$ | Y   |
|-----------|------------|--------------|-------------|-----|
| 000       | 0          | 0            | 000000      | 000 |
| 001       | 1          | 1            | 000001      | 000 |
| 010       | 2          | 4            | 000100      | 000 |
| 011       | 3          | 9            | 001001      | 001 |
| 100       | 4          | 16           | 010000      | 010 |
| 101       | 5          | 25           | 011001      | 011 |
| 110       | 6          | 36           | 100100      | 100 |
| 111       | 7          | 49           | 110001      | 110 |

6.3 62

| X   | Y   |
|-----|-----|
| 000 | 000 |
| 001 | 000 |
| 010 | 000 |
| 011 | 001 |
| 100 | 010 |
| 101 | 011 |
| 110 | 100 |
| 111 | 110 |

6.3 63

| $X_2 X_1 X_0$ | $Y_2 Y_1 Y_0$ |
|---------------|---------------|
| 000           | 000           |
| 001           | 000           |
| 010           | 000           |
| 011           | 001           |
| 100           | 010           |
| 101           | 011           |
| 110           | 100           |
| 111           | 110           |

Truth Table for  $Y_2$ :

| $X_2 \backslash X_1 X_0$ | 00 | 01 | 11 | 10 |
|--------------------------|----|----|----|----|
| 0                        | 0  | 0  | 0  | 0  |
| 1                        | 0  | 0  | 1  | 1  |

6.3 64

| $X_2 X_1 X_0$ | $Y_2 Y_1 Y_0$ |
|---------------|---------------|
| 000           | 000           |
| 001           | 000           |
| 010           | 000           |
| 011           | 001           |
| 100           | 010           |
| 101           | 011           |
| 110           | 100           |
| 111           | 110           |

Truth Table for  $Y_2$ :

| $X_2 \backslash X_1 X_0$ | 00 | 01 | 11 | 10 |
|--------------------------|----|----|----|----|
| 0                        | 0  | 0  | 0  | 0  |
| 1                        | 0  | 0  | 1  | 1  |

6.3 65

| $X_2 X_1 X_0$ | $Y_2 Y_1 Y_0$ |
|---------------|---------------|
| 000           | 000           |
| 001           | 000           |
| 010           | 000           |
| 011           | 001           |
| 100           | 010           |
| 101           | 011           |
| 110           | 100           |
| 111           | 110           |

Truth Table for  $Y_1$ :

| $X_2 \backslash X_1 X_0$ | 00 | 01 | 11 | 10 |
|--------------------------|----|----|----|----|
| 0                        |    |    |    |    |
| 1                        |    |    |    |    |

6.3 66

| $X_2 X_1 X_0$ | $Y_2 Y_1 Y_0$ |
|---------------|---------------|
| 000           | 000           |
| 001           | 000           |
| 010           | 000           |
| 011           | 001           |
| 100           | 010           |
| 101           | 011           |
| 110           | 100           |
| 111           | 110           |

| $X_2 \backslash X_1 X_0$ | 00 | 01 | 11 | 10 |
|--------------------------|----|----|----|----|
| 0                        | 0  | 0  | 0  | 0  |
| 1                        | 1  | 1  | 1  | 0  |

$Y_1$

6.3 67

| $X_2 X_1 X_0$ | $Y_2 Y_1 Y_0$ |
|---------------|---------------|
| 000           | 000           |
| 001           | 000           |
| 010           | 000           |
| 011           | 001           |
| 100           | 010           |
| 101           | 011           |
| 110           | 100           |
| 111           | 110           |

| $X_2 \backslash X_1 X_0$ | 00 | 01 | 11 | 10 |
|--------------------------|----|----|----|----|
| 0                        |    |    |    |    |
| 1                        |    |    |    |    |

$Y_0$

6.3 68

| $X_2 X_1 X_0$ | $Y_2 Y_1 Y_0$ |
|---------------|---------------|
| 000           | 000           |
| 001           | 000           |
| 010           | 000           |
| 011           | 001           |
| 100           | 010           |
| 101           | 011           |
| 110           | 100           |
| 111           | 110           |

| $X_2 \backslash X_1 X_0$ | 00 | 01 | 11 | 10 |
|--------------------------|----|----|----|----|
| 0                        | 0  | 0  | 1  | 0  |
| 1                        | 0  | 1  | 0  | 0  |

$Y_0$

6.3 69

| $X_2 \backslash X_1 X_0$ | 00 | 01 | 11 | 10 |
|--------------------------|----|----|----|----|
| 0                        | 0  | 0  | 0  | 0  |
| 1                        | 0  | 0  | 1  | 1  |

$Y_2$

| $X_2 \backslash X_1 X_0$ | 00 | 01 | 11 | 10 |
|--------------------------|----|----|----|----|
| 0                        | 0  | 0  | 0  | 0  |
| 1                        | 1  | 1  | 1  | 0  |

$Y_1$

| $X_2 \backslash X_1 X_0$ | 00 | 01 | 11 | 10 |
|--------------------------|----|----|----|----|
| 0                        | 0  | 0  | 1  | 0  |
| 1                        | 0  | 1  | 0  | 0  |

$Y_0$

6.3 70

| $X_2 \backslash X_1 X_0$ | 00 | 01 | 11 | 10 |
|--------------------------|----|----|----|----|
| 0                        | 0  | 0  | 0  | 0  |
| 1                        | 0  | 0  | 1  | 1  |

$Y_2$

| $X_2 \backslash X_1 X_0$ | 00 | 01 | 11 | 10 |
|--------------------------|----|----|----|----|
| 0                        | 0  | 0  | 0  | 0  |
| 1                        | 1  | 1  | 1  | 0  |

$Y_1$

| $X_2 \backslash X_1 X_0$ | 00 | 01 | 11 | 10 |
|--------------------------|----|----|----|----|
| 0                        | 0  | 0  | 1  | 0  |
| 1                        | 0  | 1  | 0  | 0  |

$Y_0$

$Y_2 = X_1 X_2$   
 $Y_1 = X_1' X_2 + X_0 X_2$   
 $Y_0 = X_0 X_1 X_2' + X_0 X_1' X_2$

6.3 71

**Remark**

A remark on  $Y_0$ .

The expression can be factorized as it follows:

$$Y_0 = X_0 X_1 X_2' + X_0 X_1' X_2 = X_0 (X_1 X_2' + X_1' X_2) = X_0 (X_1 \oplus X_2)$$

6.3 72

**Remark (cont'ed)**

The same expression could be easily obtained by a proper cover of the  $Y_0$  K-map:

6.3

73

**Remark (cont'ed)**

|       |           |    |    |    |    |
|-------|-----------|----|----|----|----|
|       | $X_1 X_0$ | 00 | 01 | 11 | 10 |
| $X_2$ | 0         | 0  | 0  | 1  | 0  |
|       | 1         | 0  | 1  | 0  | 0  |

$Y_0$

6.3

74

**Remark (cont'ed)**

|       |           |    |    |    |    |
|-------|-----------|----|----|----|----|
|       | $X_1 X_0$ | 00 | 01 | 11 | 10 |
| $X_2$ | 0         | 0  | 0  | 1  | 0  |
|       | 1         | 0  | 1  | 0  | 0  |

$Y_0$

=

|       |           |    |    |    |    |
|-------|-----------|----|----|----|----|
|       | $X_1 X_0$ | 00 | 01 | 11 | 10 |
| $X_2$ | 0         | 1  | 0  | 1  | 0  |
|       | 1         | 0  | 1  | 0  | 1  |

A

∧

|       |           |    |    |    |    |
|-------|-----------|----|----|----|----|
|       | $X_1 X_0$ | 00 | 01 | 11 | 10 |
| $X_2$ | 0         | 0  | 1  | 1  | 0  |
|       | 1         | 0  | 1  | 1  | 0  |

B

6.3

75

**Remark (cont'ed)**

|       |           |    |    |    |    |
|-------|-----------|----|----|----|----|
|       | $X_1 X_0$ | 00 | 01 | 11 | 10 |
| $X_2$ | 0         | 0  | 0  | 1  | 0  |
|       | 1         | 0  | 1  | 0  | 0  |

$Y_0$

=

|       |           |    |    |    |    |
|-------|-----------|----|----|----|----|
|       | $X_1 X_0$ | 00 | 01 | 11 | 10 |
| $X_2$ | 0         | 1  | 0  | 1  | 0  |
|       | 1         | 0  | 1  | 0  | 1  |

A

∧

|       |           |    |    |    |    |
|-------|-----------|----|----|----|----|
|       | $X_1 X_0$ | 00 | 01 | 11 | 10 |
| $X_2$ | 0         | 0  | 1  | 1  | 0  |
|       | 1         | 0  | 1  | 1  | 0  |

B

$Y_0 = A B = (X_0 \oplus X_1 \oplus X_2) X_0 = (X_1 \oplus X_2) X_0$

